

Truth Table $\rightarrow$ Boolean Expression $\rightarrow$ Circuit
2's complement

lsb of 1's complement + 1

$$\begin{array}{r} 101011 \rightarrow 010100 \\ +1 \\ \hline 010101 \end{array}$$

10101 $\xrightarrow{2's}$ 01011 [lsb ko 1 se badh kar 1's complement] $\downarrow$ 1's

$$\begin{array}{r} 01010 \\ +1 \\ \hline 01011 \end{array}$$

So, this process is not universal.

10100 $\xrightarrow{2's}$ 01010
 $\downarrow$ 1's
 01011
 $+1$
 $\hline$
 01100


Not correct

General process: lsb se badh kar 1's complement apply karna hai. jab tak bit 0 hai, usko 0 hi rakhte hain aur jab 1 aata hai, usko 0 kar dete hain aur uske baad ke bits ko 1 kar dete hain.

$$\begin{array}{r} 10100 \rightarrow 9 \text{ intakt} \\ \downarrow 2's \\ 01100 \end{array}$$

H.W. rth complement

2's complement hai negative number ke liye use kiya jata hai. $9 - 2's = -9$

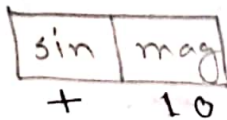MSB $\rightarrow$ sign1 $\rightarrow$ negative0 $\rightarrow$ positiveTotal combinations: 2^n [n = no. of bit]

2's complement form for signed numbers:

$$-(2^{n-1}) \text{ to } +(2^{n-1} - 1)$$

$$n=8, -(2^{8-1}) = -128 \text{ (minimum)}$$

$$+(2^{8-1} - 1) = +127 \text{ (maximum)}$$

$$1k = 2^{10}$$

$$10000000 = 128 \text{ (unsigned)}$$

$$= -128 \text{ (signed)}$$

MSB = 1 & other bits = 0 $\Rightarrow$ signed & unsigned $\Rightarrow$ binary representation same $\Rightarrow$ 1

signed $\xrightarrow{2's}$ magnitudeuniversal $\Rightarrow$ BCD to 4 bit use $\Rightarrow$ 1

*BCD to Binary

BCD Addition

$$369 \rightarrow 0011 \ 0110 \ 1001$$

$$245 \rightarrow 0010 \ 0100 \ 0101$$

$$\hline 614 \quad 0101 \ 1010 \ 1110$$

 $\downarrow$

5

10

14

 $\rightarrow$ representation

$$0110 \ 0001 \ 0100$$

$$0110$$

$$0110$$

$$\hline 0110 \ 0001 \ 0100$$

6

1

4

9 $\Rightarrow$ carry $\Rightarrow$ 27, correction needed

highest possible using 4 bit = 1111


but highest possible in 8421 = 1001

sub: $0110 \rightarrow 6$

That is why, Addition of 6 is done to the output, as 4 bit is not enough, that's why 0110 add is done.

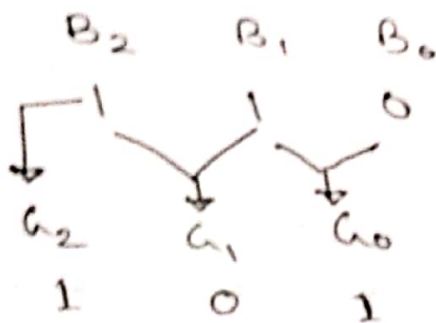17.10.2022


Binary to Gray $\rightarrow$ diff consecutive bit is difference & MSB remains same.



B_1	B_0	Diff
0	0	0
1	0	1
0	1	1
1	1	0

which turns out to be an Ex-OR gate principle.

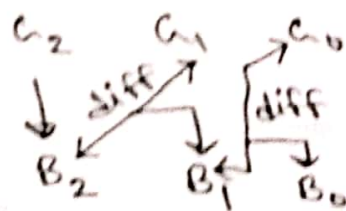Gray to Binary $\rightarrow$ same output as input because use same logic.



ASCII code $\rightarrow$ basic: 7 bit
used to: 8 bit

application
keyboards $\rightarrow$

Error detection $\rightarrow$ odd parity bit error
transmission or use
can be 1

Parity bit

$\rightarrow$ odd (0, 1)
 $\rightarrow$ even (0, 1)

7 6 5 4 3 2 1 0
1 0 0 1 1 0 0 1
Even parity

Even method: 3 bits 1 আছে, তাই even করে
করে 1 পাঠাবে।

যদি even number of 1 থাকে, তাহা
parity bit 0 রহবে।

18.10.2022

Logic 0 (Typical 0 ~ 0.8 V)

Logic 1 (Typical 2.4 ~ 5 V)

variable $\rightarrow 2 \rightarrow 2^n$ entries

variable $\rightarrow n \rightarrow 2^n$ entries

$X = AB$
 $X = A \cdot B$ } AND


$$1 + X + Y + Z + P = 1 + 0 = 1$$

$$1. X = X$$


$$X + \bar{X} = 1$$


$$X \cdot \bar{X} = 0$$

#

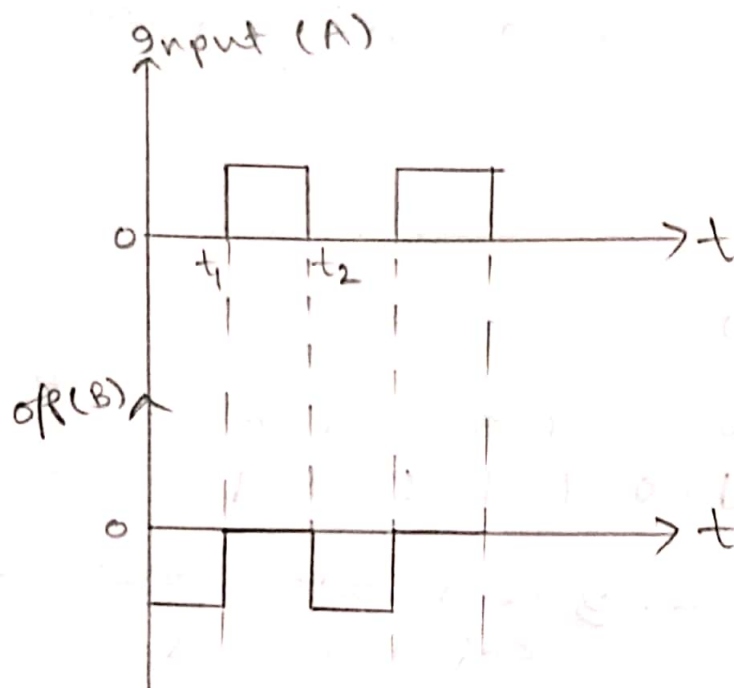

#

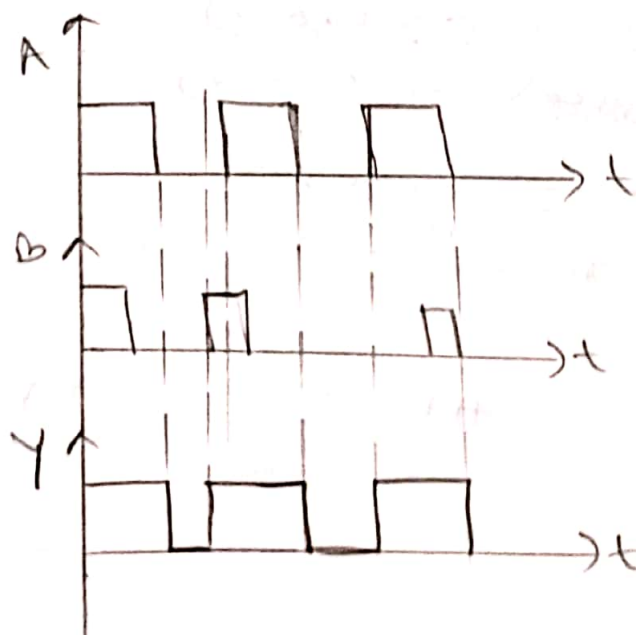

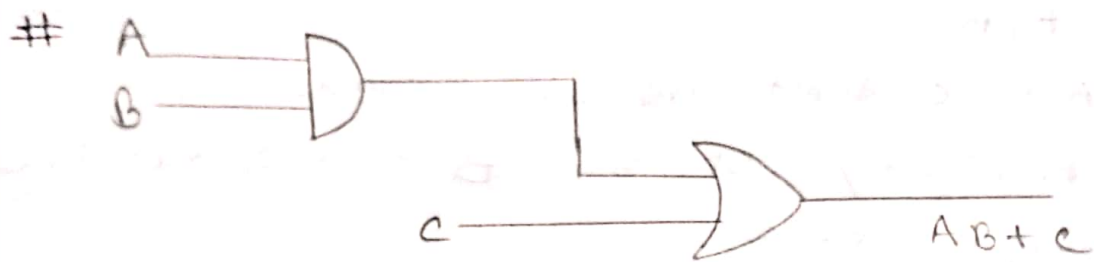

When will be the circuit activated?

→

$$A = 1$$

$$B = 1$$

$$AB = 1$$

$$AB + C = 1 + 0 = 1$$

$$C = 0, 1$$

$$AB + C = 1 + 1 = 1$$

i. $A = 1, B = 1, C = 0$

$$A = 1, B = 1, C = 1$$

ii. $A = 0, B = 1, AB = 0, C = 1, AB + C = 0 + 1 = 1$

$$A = 1, B = 0, AB = 0, C = 1, AB + C = 1$$

Input			Output
A	B	C	$Y = AB + C$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

i. $C \rightarrow \text{high}$
ii. $A \& B \rightarrow \text{both high}$

Fan A, B, C

i) A, B, C don't ON at a time


ii) A always ON but B and C not ON at a time.

Input			Output	
A	B	C	Y	
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	0	1


i) Three input circuits

ii) Circuit Activates when majority inputs are activated.

#

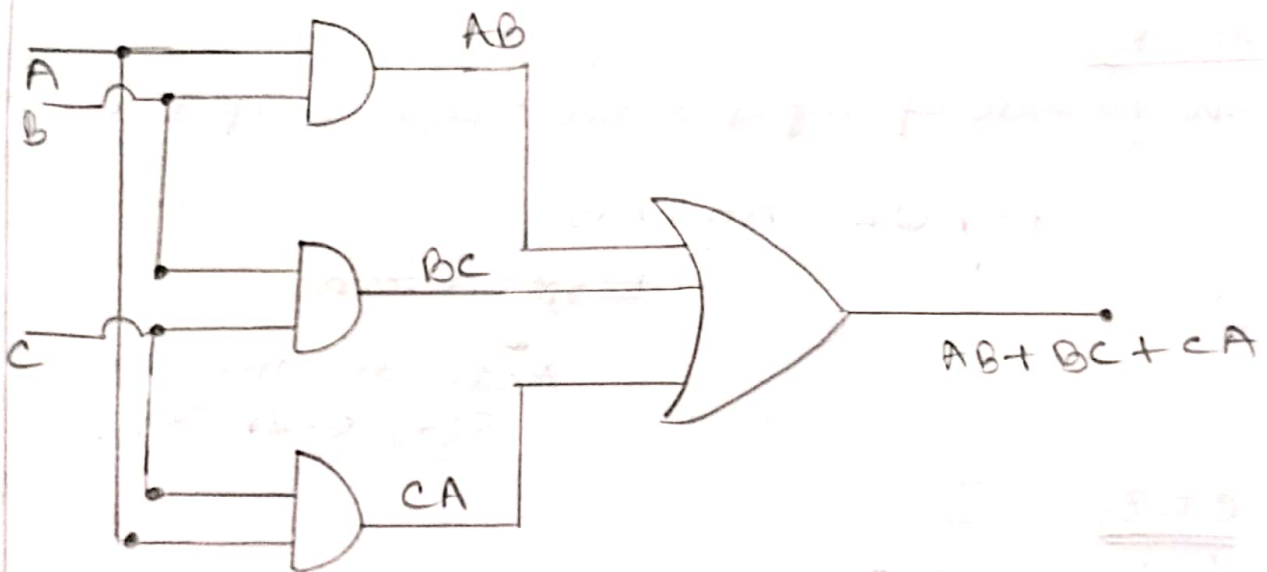
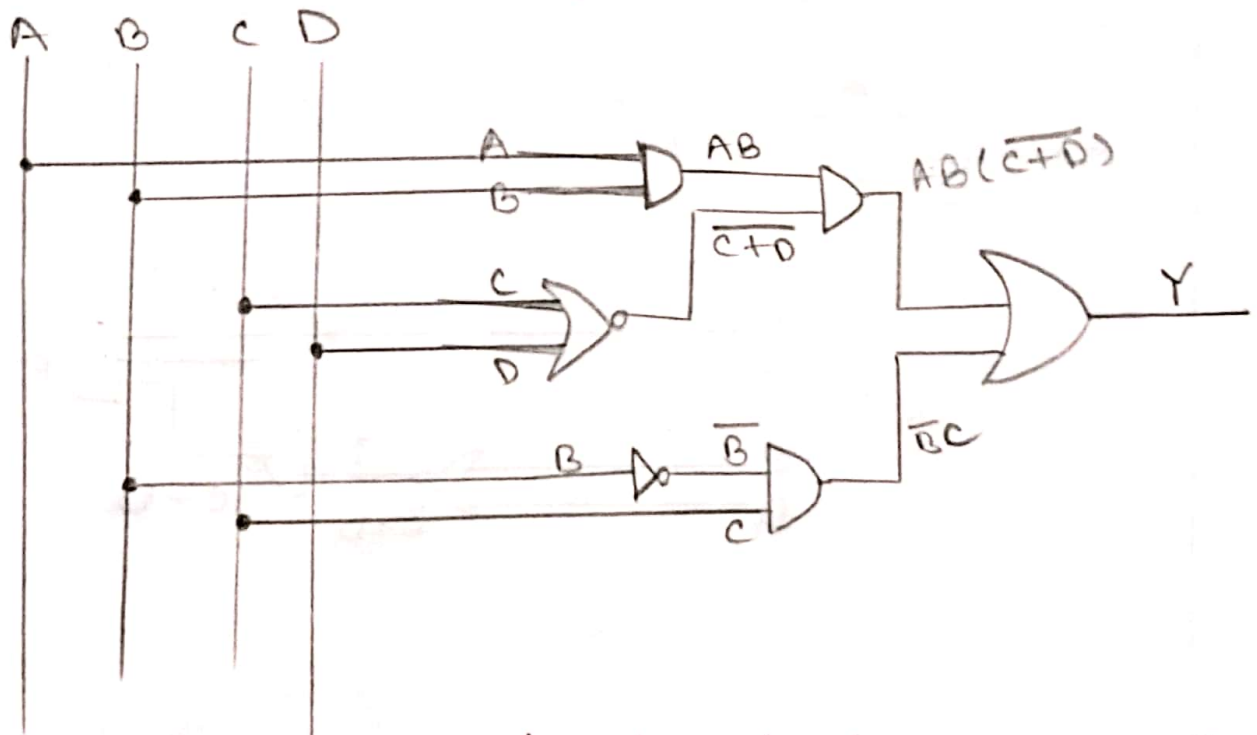
$$\# Y = \underbrace{AB(\overline{C+D})}_{P_1} + \underbrace{\overline{B}C}_{P_2}$$



3 input gate is more expensive than 2 input gate.

NAND
NOR } Universal Gate

Ex-OR

000 number of input active 2kaar, output active.

$$Y = A \oplus B = \bar{A}B + A\bar{B}$$

→ minterm

↓
Activate gate or
or gate or


CT-01

Lecture: 1, 2, 3

24.10.2022

$$\# Y = \overline{AB \cdot (C+D)}$$

Implement by NOR and NAND gate.

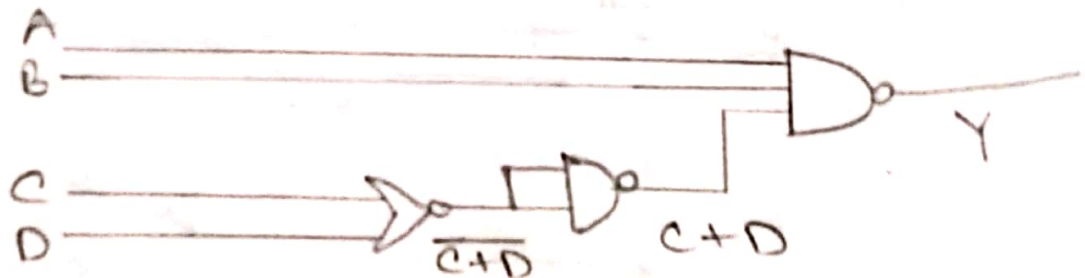

$Y = \overline{AB(C+D)}$, only NOR gate.

Boolean Theorem is not vector dependent.


$Y = a + \bar{a}b$. simplify the expression.

$$\begin{aligned} Y &= a + \bar{a}b \\ &= a \cdot 1 + \bar{a}b \\ &= a(1+b) + \bar{a}b \\ &= a + ab + \bar{a}b \\ &= a + b(a + \bar{a}) \\ &= a + b \cdot 1 \\ &= a + b \end{aligned}$$

$$\begin{aligned} 1+x &= 1 \\ x+\bar{x} &= 1 \\ x \cdot \bar{x} &= 0 \\ x \cdot x &= x \end{aligned}$$

$$a + \bar{a}b = a + b$$

De Morgan's Theorem

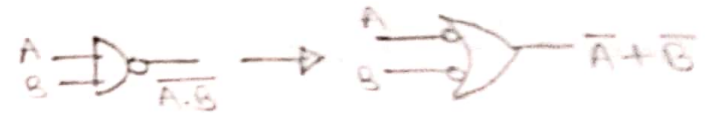i. $\overline{x \cdot y} = \bar{x} + \bar{y}$ 

ii. $\overline{x + y} = \bar{x} \cdot \bar{y}$




NAND / universal gate

NAND gate as universal gate


1. NAND gate as NOT



2. NAND gate as AND

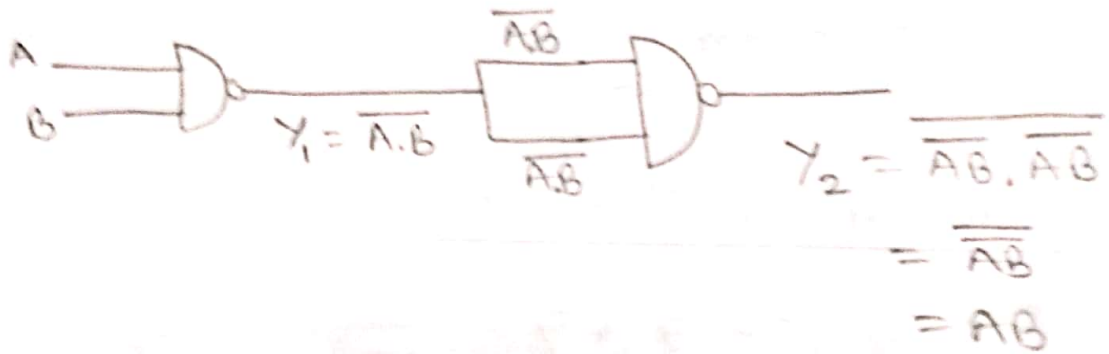

3. NAND gate as OR

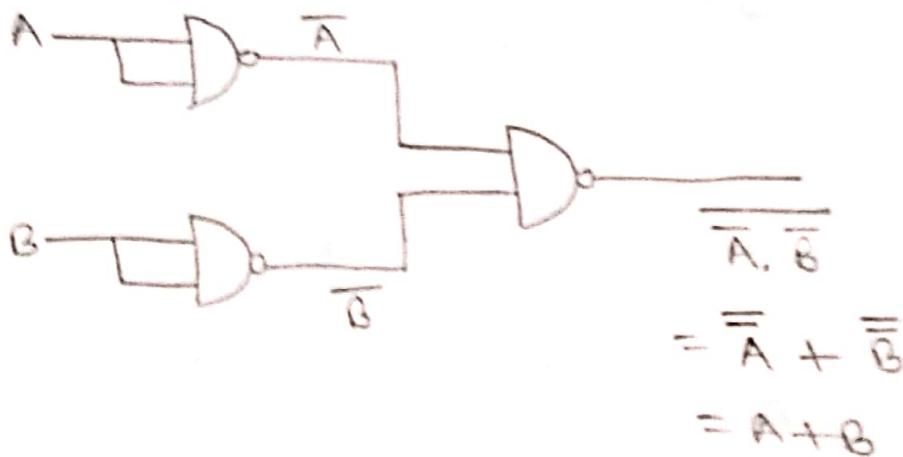



Inversion bubble

Active - high $\rightarrow$ power dissipation (less).
That's why Active - low $\rightarrow$ zero not preferable
(i.e., NOR, NAND gate first)!



$$\overline{A+B} = \overline{\overline{\overline{A+B}}} = \overline{\overline{A} \cdot \overline{B}} = \overline{\overline{A} \cdot \overline{B}}$$

Canonical & Standard forms

$Y = \overline{A}B + AB \rightarrow$ sum of product (SOP) $\rightarrow m$

$Y = (A+B) \cdot (A+\overline{B}) \rightarrow$ Product of sum
(POS) $\rightarrow M$

Canonical form $\rightarrow$ minimize $\rightarrow$ or or
form $\rightarrow$ or or

variable $\rightarrow 0 \rightarrow$ product term $\rightarrow$ minterm $\rightarrow$ complementary
 $\rightarrow 1 \rightarrow$ product sum $\rightarrow$ maxterm $\rightarrow$ complementary

x	y	z	Minterm	maxterm
0	1	1	$x'y'z$	$x + y' + z'$

$$Y_1 = x'y'z' + xyz$$

$$= m_0 + m_7$$

$$Y_1(x, y, z) = \sum(0, 7) \rightarrow \text{Function Representation}$$

$$Y_2 = (x + y + z)(x' + y' + z')$$

$$= M_0 \cdot M_7$$

$$Y_2(x, y, z) = \prod(0, 7)$$

Variable ke minterm/maxterm ko prkash karke
 OR, decimal ko convert karke hai. OR
 ke decimal. uske m/M ko suffix.

m = minterm

M = maxterm

Σ = for m

Π = for M

#

A	B	C	F	Min(F)	Max(F)
0	0	0	1	$\bar{A}\bar{B}\bar{C}$	
0	0	1	1	$\bar{A}\bar{B}C$	
0	1	0	0		$A\bar{B}\bar{C}$
0	1	1	1	$\bar{A}BC$	
1	0	0	1	$A\bar{B}\bar{C}$	
1	0	1	0		$A\bar{B}C$
1	1	0	1	$AB\bar{C}$	
1	1	1	0		$AB+C$

$$\rightarrow F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + AB\bar{C}$$

(using minterm)

$$F = (A + \bar{B} + C) \cdot (\bar{A} + B + \bar{C}) \cdot (\bar{A} + \bar{B} + \bar{C})$$


(using maxterm)

$F=1$ રહ્યું, minterm એ પ્રકાશ કર્યું છે અને

$F=0$ " , maxterm " " " "

But ફરક છે- મિન્ટર્મ અને મેક્સર્મ એકસરખા, ભેદભાગ
અર્થે ઉભા કરવામાં આવે છે. અહીં simplify
કરવું છે. maxterm એ simplification કર
tough.

$$\begin{aligned} \rightarrow F_{\min} &= \bar{A}\bar{B}(\bar{C} + C) + A\bar{C}(\bar{B} + B) + \bar{A}BC \\ &= \bar{A}\bar{B} + \bar{A}BC + A\bar{C} \\ &= \bar{A}(\bar{B} + BC) + A\bar{C} \\ &= \bar{A}(\bar{B} + C) + A\bar{C} \\ &= \bar{A}\bar{B} + \bar{A}C + A\bar{C} \\ &= \bar{A}\bar{B} + A \oplus C \\ &= \overline{\overline{\bar{A}\bar{B}}} + A \oplus C \\ &= \overline{\bar{A} + \bar{B}} + A \oplus C \\ &= \overline{A + B} + A \oplus C \end{aligned}$$

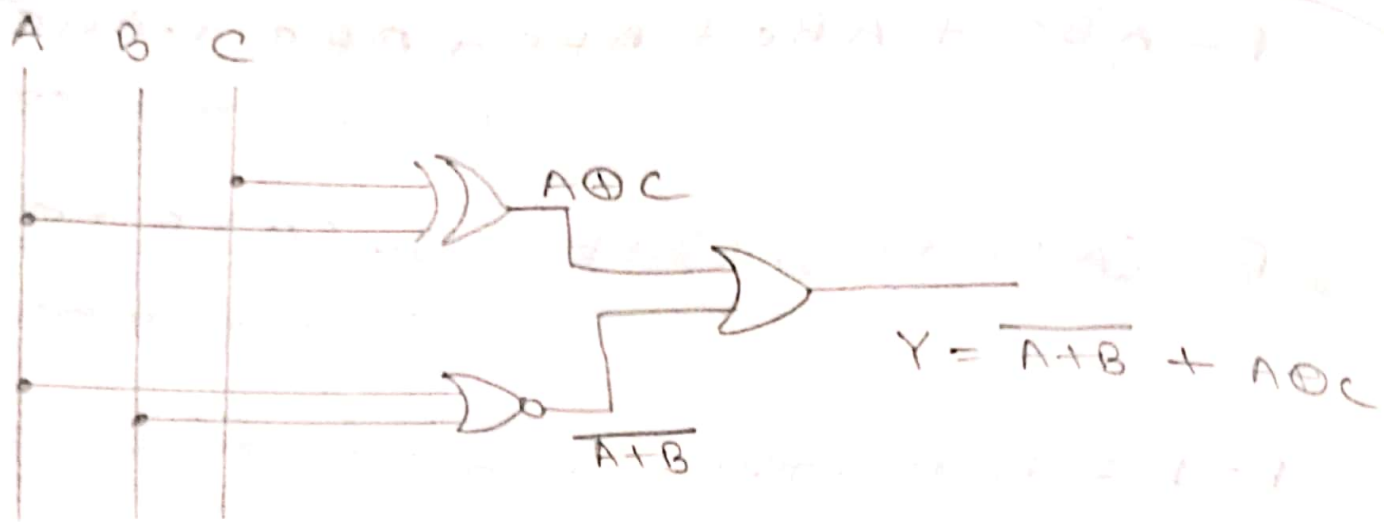

$$\begin{aligned}
 \# \quad Y &= AB + BC + CA \\
 &= AB(C + \bar{C}) + BC(A + \bar{A}) + CA(B + \bar{B}) \\
 &= ABC + AB\bar{C} + ABC + \bar{A}BC + ABC + A\bar{B}C \\
 &= ABC + AB\bar{C} + \bar{A}BC + A\bar{B}C \\
 &= m_7 + m_6 + m_3 + m_5
 \end{aligned}$$

$$Y(A, B, C) = \Sigma(3, 5, 6, 7)$$

standard form contains all the variables.

$$\begin{aligned}
 \# \quad Y &= A(B + C) \\
 &= (A + 0 + 0) \cdot (0 + B + C) \\
 &= (A + B\bar{B}) (A\bar{A} + B + C) \\
 &= (A + B)(A + \bar{B})(A + B + C)(\bar{A} + B + C) \\
 &= (A + B + C\bar{C})(A + \bar{B} + C\bar{C})(\bar{A} + B + C)(A + B + C) \\
 &= (A + B + C)(A + B + \bar{C})(A + \bar{B} + C)(A + \bar{B} + \bar{C}) \\
 &\quad (A + B + C)(\bar{A} + B + C)
 \end{aligned}$$

$$= (A+B+C)(A+B+\bar{C})(A+\bar{B}+C)(A+B+\bar{C})(A+\bar{B}+\bar{C})$$

$$f(A, B, C) = \Pi(0, 1, 2, 3, 4)$$

$$\# y = A + BC$$

generate the function for maxterm.
(though it's in minterm Σ)

→ Minterm ko Σ se, Σ ko Π se term nikalke
output maxterm.

$$\begin{aligned} y = A + BC &= A(B + \bar{B}) + BC(A + \bar{A}) \\ &= AB + A\bar{B} + ABC + \bar{A}BC \\ &= ABC + AB\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + ABC + \bar{A}BC \\ &= ABC + \bar{A}BC + A\bar{B}C + AB\bar{C} + A\bar{B}\bar{C} \end{aligned}$$

↓
minterm

$$\therefore y(A, B, C) = \Sigma(3, 4, 5, 6, 7)$$

$$\therefore y(A, B, C) = \Pi(0, 1, 2)$$

$$\Rightarrow y = (A+B+C) \cdot (A+\bar{B}+\bar{C}) \cdot (A+\bar{B}+C)$$

↑
maxterm

Karnaugh Map / K-Map

Karnaugh Maps (K-maps)

$$Y = ABC + ABC + ABC + ABC$$

$$= AB + BC + CA$$

$$= \text{EX-OR}$$

> Both are correct

k-map gives optimal solution পাওয়া যায়।

2-variable k-maps

$$AB + A\bar{B}$$

$$= A(B + \bar{B})$$

$$= A$$

no. of var = 2

$\therefore$ subcells = $2^2 = 4$

সমস্ত combination হয়, - সমস্ত subcell
হয় k-map এ।

$$\text{subcell} = 2^n$$

n = no. of variable

		B	
		0	1
A	0	00	01
	1	10	11

mapping of 2-var

		BC			
		00	01	11	10
A	0	000	001	011	010
	1	100	101	111	110

Mapping of 3-var.

$$\text{subcell}, 2^3 = 8$$

Input output

A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

variable = 2

sub-cell = $2^2 = 4$

	0	1
0	0	1
1	1	1

ଆବଶ୍ୟକ loop ଏ ସଂଖ୍ୟା

1 ଆବଶ୍ୟକ ପାର୍ଥକ୍ୟ $\rightarrow 2^n$

$$= 2^n(0, 1, 2)$$

$$= 2^0, 2^1, 2^2$$

$$= 1, 2, 4$$

ଆବଶ୍ୟକ 2ଟି
ଆବଶ୍ୟକ 3ଟି

invalid as we have only 3 is here.

$$\therefore f(A, B) = A + B$$

#

	0	1
00	0	1
01	0	1
11	0	1
10	0	1

max No. of one in a loop,

$$= 2^3$$

$$= 2^0, 2^1, 2^2, 2^3$$

invalid

→ 1s should be adjacent.

→ loop continues until one 1 is outside the loop.

3-variable k-maps

#

		A	
		0	1
Bc	00	1	1
	01	0	1
	11	0	0
	10	1	1

open loop $\rightarrow$ AB change
 શરૂ, but c fixed થાય છે.

$$c = 0$$

So, એ 4 બંધ 1 adjacent.

$$\therefore Y = \bar{c}$$

#

		A	
		0	1
Bc	00	1	1
	01	0	1
	11	0	0
	10	1	1

$\rightarrow$ એ single (એક માત્ર)

So, એ 2' = 2 બંધ adjacent

નિમ્ન loop બંધ.

$$\therefore A\bar{B}$$

$$\therefore Y = \bar{c} + A\bar{B}$$

મતિ 2 બંધ adjacent 3 માં
 આવે, ત્યારે 2' = 1 બંધ one નિમ્ન
 બંધ થાય.

$F = \Sigma(0, 1, 3, 7) \rightarrow$ minimum 3 variable
 એ map થાય.

		c	
		0	1
AB	00	1 ₀₀₀	1 ₀₀₁
	01	0 ₀₁₀	1 ₀₁₁
	11	0 ₁₁₀	1 ₁₁₁
	10	0 ₁₀₀	0 ₁₀₁

$\rightarrow \bar{A}\bar{B}$

		A	
		0	1
Bc	00	1 ₀₀₀	0 ₁₀₀
	01	1 ₀₀₁	0 ₁₀₁
	11	1 ₀₁₁	1 ₁₁₁
	10	0 ₀₁₀	0 ₁₁₀

$\rightarrow BC$

$\rightarrow BC$

$$Y = \bar{A}\bar{B} + BC$$

$$Y = \bar{A}\bar{B} + BC$$

2 નિમ્ન same answer નાથે, So, k-map is giving
 the optimal solution.

#

		A	
		0	1
B	C	00	1
		01	1
		11	1
		10	0

k-map

minterm,

$$F = \bar{A}\bar{B} + \bar{A}C + \bar{B}C$$

$F(a,b,c) = \bar{a}c + abc + b\bar{c}$

↑
MSB

$$= \bar{a}c(b+\bar{b}) + abc + b\bar{c}(a+\bar{a})$$

unless otherwise stated.

$$= \bar{a}bc + \bar{a}\bar{b}c + abc + a\bar{b}\bar{c} + \bar{a}b\bar{c}$$

$$= \Sigma(3, 1, 7, 6, 4)$$

$$= \Sigma(1, 2, 4, 6, 7)$$

		A	
		0	1
B	C	00	0
		01	1
		11	1
		10	1

k-map

$$F = B + \bar{A}C$$

4th Adjacent 1 is
only A and C is value
variable is 0, only
B.

and 2 is 1 is only
change is, only
AC.

#

		A	
		0	1
bc	00	1	0
	01	0	1
	11	1	0
	10	0	1

$$F = \bar{A}\bar{B}\bar{C} + A\bar{B}C + \bar{A}BC + AB\bar{C}$$

k-map complex gate or minimization or
or or

$$F = (\bar{A}\bar{B}\bar{C} + \bar{A}BC) + (A\bar{B}C + AB\bar{C})$$

$$= \bar{A}(\bar{B}\bar{C} + BC) + A(\bar{B}C + B\bar{C})$$

$$= \bar{A}(\overline{B \oplus C}) + A(B \oplus C)$$

$$= \bar{A}\bar{x} + Ax$$

$$= \overline{A \oplus x}$$

$$= \overline{A \oplus (B \oplus C)}$$

$$B \oplus C = x$$



Design a full Adder.

Input			Output	
A	B	C	C ₀	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

k-map for carry:

		A		
		0	1	
BC	00	0	0	4
	01	0	1	5
	11	1	1	7
	10	0	1	6

$$\text{carry} = BC + AC + AB$$

k-map for sum:

		A		
		0	1	
BC	00	0	1	4
	01	1	0	5
	11	0	1	7
	10	1	0	6

$$\text{sum} = A\bar{B}\bar{C} + \bar{A}\bar{B}C + ABC + \bar{A}B\bar{C}$$

$$\text{Sum} = A(\bar{B}\bar{C} + BC) + \bar{A}(\bar{B}C + B\bar{C})$$

$$= A(\overline{B \oplus C}) + \bar{A}(B \oplus C)$$


$$= \cancel{A \oplus (B \oplus C)} + \cancel{A \oplus (B \oplus C)}$$

$$= A \cdot \bar{x} + \bar{A} \cdot x$$



$$= A \oplus x$$

$$= A \oplus (B \oplus C)$$

$$x = B \oplus C$$

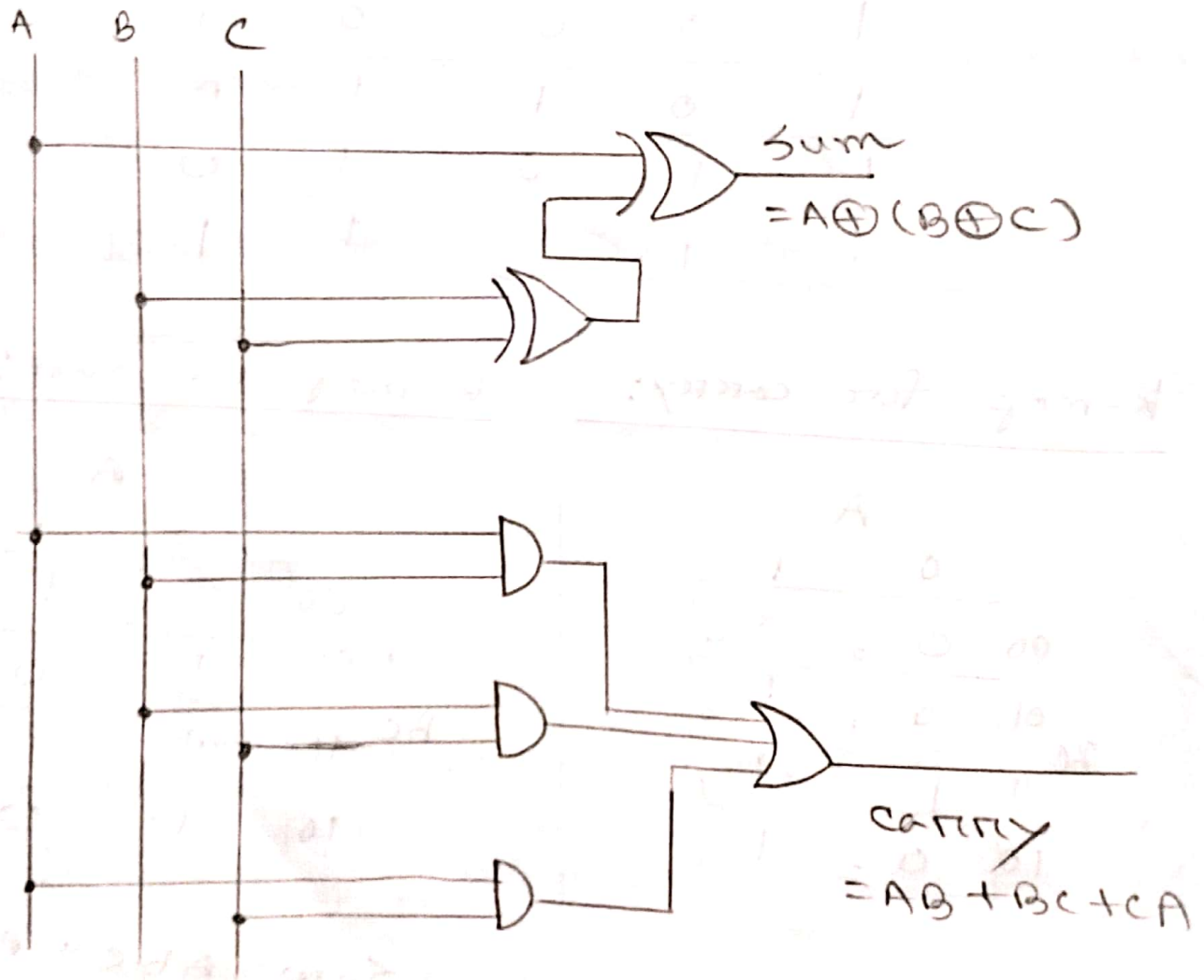


#

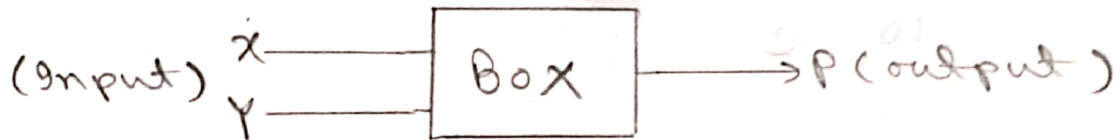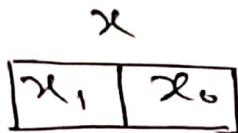

1. If both strings are in activates.

2. " " " " deactivates.

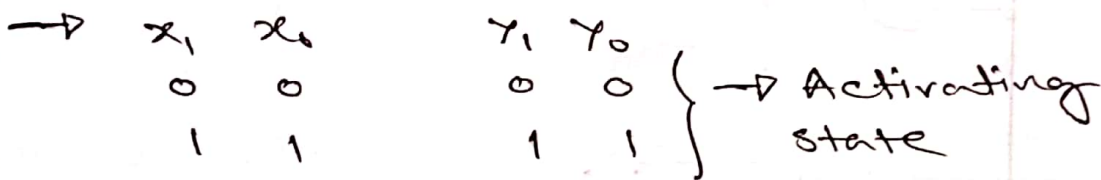


Design a three input logic circuit whose output will be high when majority of inputs are in high condition.

A	B	C	Y
0	0	0	0
0	1	1	1
1	0	0	0
1	1	1	1
0	0	1	0
0	1	0	0
1	0	1	1
1	1	0	1


	A	
	0	1
BC	00	0
	01	0
	11	1
	10	0

$$Y = AC + BC + AB$$

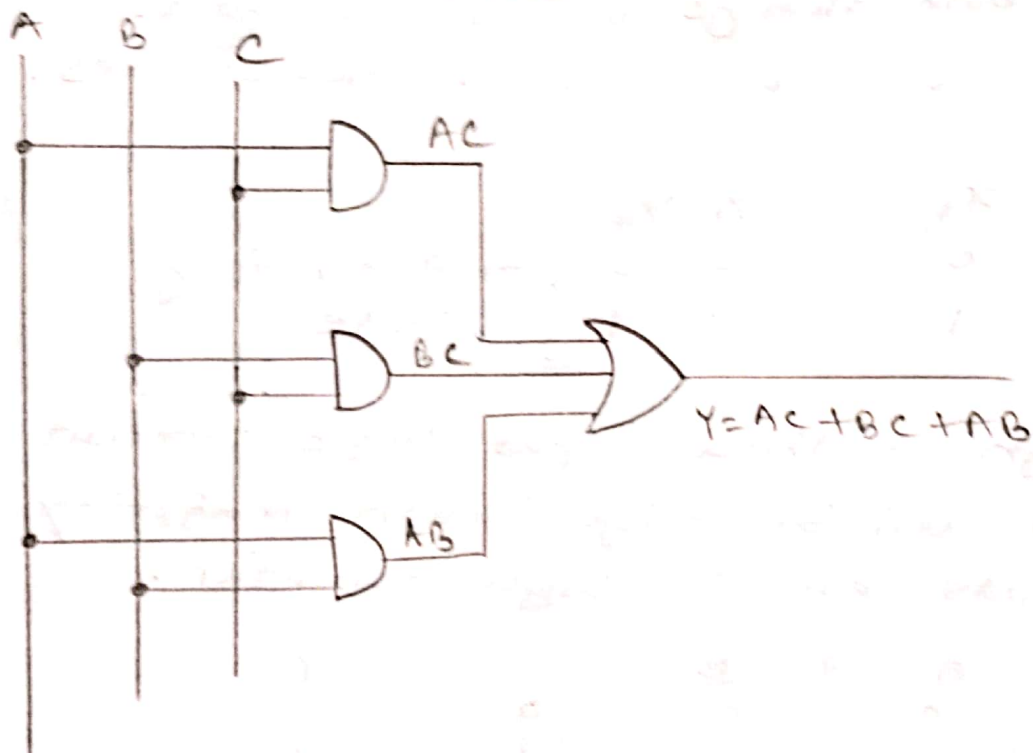

using only universal gate,
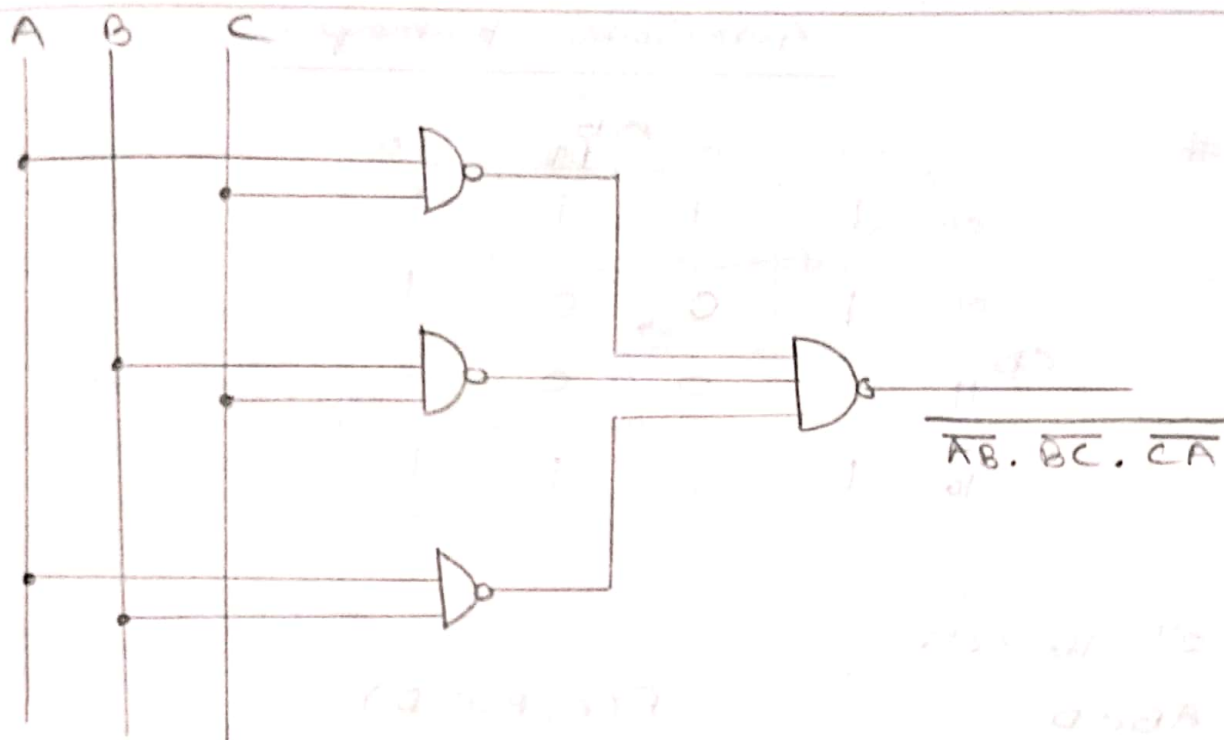
$$\begin{aligned}
 Y &= AC + BC + AB \\
 &= \overline{\overline{AC + BC + AB}} \\
 &= \overline{\overline{AC} \cdot \overline{BC} \cdot \overline{AB}} \\
 &\text{# } \overline{\overline{AC} \cdot \overline{BC} \cdot \overline{AB}}
 \end{aligned}$$




using only NOR gate, (minimum number of gate)

$$Y = AB + BC + CA$$

H.W

$$= \overline{\overline{A} \cdot \overline{B}} + \overline{\overline{B} \cdot \overline{C}} + \overline{\overline{C} \cdot \overline{A}}$$
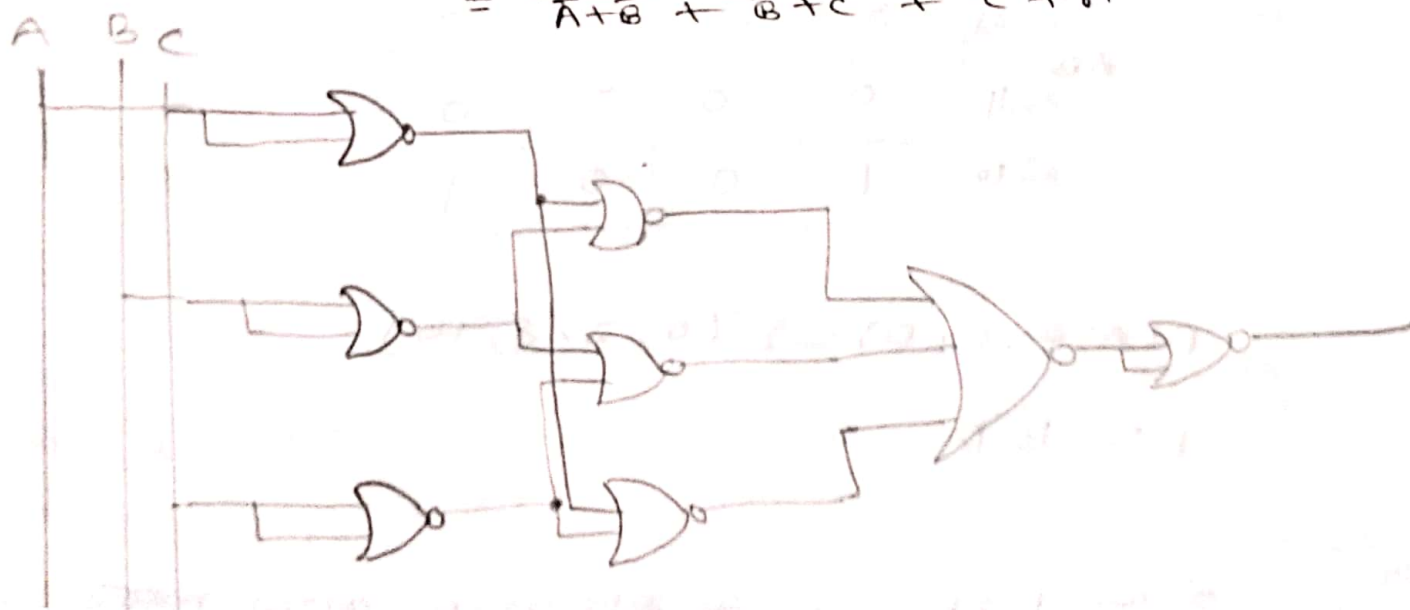
$$\neq \overline{A+B} = \overline{\overline{A+B}} = \overline{\overline{A+B}} = \overline{\overline{A+B}} = \overline{\overline{A+B}}$$



08.11.2022

4-Variable K-map

#

		AB			
		00	01	11	10
CD	00	1	1	1	1
	01	1	0	0	1
	11	1	0	0	1
	10	1	1	1	1

$2^4 = 16$ cell

ABCD
 ↓ ↓
 MSB LSB

$F(A, B, C, D)$

$= \Sigma (0, 1, 2, 3, 4, 6, 8, 9, 10, 11, 12, 14)$

$$F = \overline{B} + \overline{D}$$

#

		00	01	11	10
AB	$\overline{A}\overline{B}$ 00	1	0	0	1
	$\overline{A}B$ 01	0	0	0	0
	$A\overline{B}$ 11	0	0	0	0
	AB 10	1	0	0	1

$F(A, B, C, D) = \Sigma (0, 2, 8, 10)$

$$F = \overline{B}\overline{D}$$

2^n में 1 में 1 loop में बाँट सकते हैं, अतः नया variable eliminate करें।

$$\# F(A, B, C, D) = \pi(5, 7, 13, 15)$$

↳ max term

		C+D			
		0+0	0+1	1+1	1+0
A+B	0+0	1 0	1 1	1 3	1 2
	0+1	1 4	0 5	0 7	1 6
	1+1	1 12	0 13	0 15	1 14
	1+0	1 8	1 9	1 11	1 10

$$F = \overline{B} + \overline{D}$$

5-variable k-map (A, B, C, D, E)

A=0

		DE			
		00	01	11	10
BC	00	1 0	0 1	0 3	1 2
	01	0 4	0 5	0 7	0 6
	11	0 12	0 13	0 15	0 14
	10	1 8	0 9	0 11	1 10

A=1

		DE			
		00	01	11	10
BC	00	1 16	0 17	0 19	1 18
	01	0 20	0 21	0 23	0 22
	11	0 28	0 29	0 31	0 30
	10	1 24	0 25	0 27	1 26

$$F = \overline{C} \overline{E}$$

Don't care function

$$F(A, B, C, D)$$

$$= \Sigma(1, 3, 5, 7, 9, 13, 15)$$

$$d(A, B, C, D)$$

$$= \Sigma(0, 4, 10, 11)$$

		AB			
		00	01	11	10
CD	00	X 0	X 4	0 12	0 8
	01	1 1	1 5	1 13	1 9
	10	1 3	1 7	1 15	1 11
	11	0 2	0 6	0 14	0 10

→ 12, 13 better

don't care as function as map variables can
map as can be 0 or 1, main fun as
0 or 1 as 0 or 1.

don't care function's input either be 0
or 1 depending on personal use.

main function as simply 0/1
value as 0 or 1.

problem d, f draw map design
map, draw map design as
for looping (don't care as value 0/1).


CT-02 : lec-4,5 (till don't care)

21.11.2022

Design a logic circuit that is to produce
a High output when the voltage (represented
by a four-bit binary number ABCD)
is greater than 6 V.

Voltage				0/1
A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	1	1	1	1

→ 7

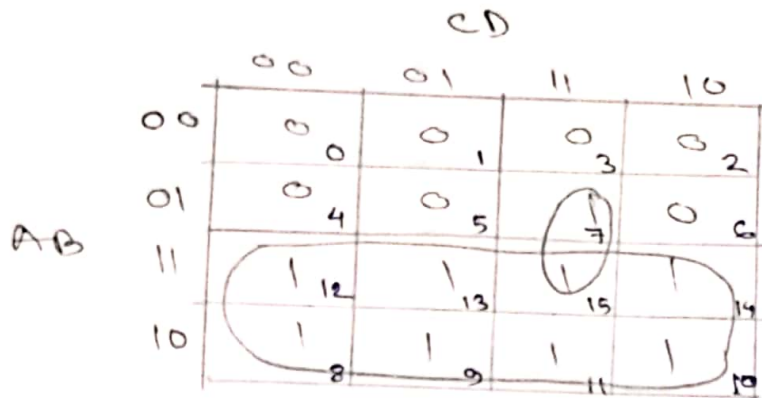

$$F = A + BCD$$



Ex. 7 (slide-5)

A	B	C	D	F		
0	0	0	0	1	$\overline{A}\overline{B}\overline{C}\overline{D}$	
0	0	0	1	1	$\overline{A}\overline{B}\overline{C}D$	
0	0	1	0	1	$\overline{A}\overline{B}C\overline{D}$	
0	0	1	1	1	$\overline{A}\overline{B}CD$	
0	1	0	0	1	$\overline{A}B\overline{C}\overline{D}$	
0	1	0	1	0		$A + \overline{B} + \overline{C} + \overline{D}$
0	1	1	0	0		$A + \overline{B} + \overline{C} + D$
0	1	1	1	0		$A + \overline{B} + \overline{C} + \overline{D}$
1	0	0	0	1	$A\overline{B}\overline{C}\overline{D}$	
1	0	0	1	1	$A\overline{B}\overline{C}D$	
1	0	1	0	0		$\overline{A} + B + \overline{C} + D$

1	0	1	1	0		$\bar{A} + B + \bar{C} + \bar{D}$
1	1	0	0	1	$AB\bar{C}\bar{D}$	
1	1	0	1	0		$\bar{A} + \bar{B} + C + \bar{D}$
1	1	1	0	0		$\bar{A} + \bar{B} + \bar{C} + D$
1	1	1	1	0		$\bar{A} + \bar{B} + \bar{C} + \bar{D}$

$$F = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D$$

		CD			
		00	01	11	10
AB	00	1	1	1	1
	01	1	0	0	0
	11	1	0	0	0
	10	1	1	0	0

$$F = \bar{A}\bar{B} + \bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}$$

Simplify the following expression.


$$\begin{aligned}
 F &= \overline{AB} + AC + \overline{A}BC \\
 &= \overline{AB} \cdot \overline{AC} + \overline{A}BC \\
 &= (\overline{A} + \overline{B}) \cdot (\overline{A} + \overline{C}) + \overline{A}BC \\
 &= \overline{A}\overline{A} + \overline{A}\overline{B} + \overline{A}\overline{C} + \overline{B}\overline{C} + \overline{A}BC \\
 &= \overline{A} + \overline{A}\overline{B}(1+C) + \overline{C}(\overline{A} + \overline{B}) \\
 &= \overline{A} + \overline{A}\overline{B} + \overline{A}\overline{C} + \overline{B}\overline{C} \\
 &= \overline{A} + \overline{A}(1+\overline{B}) + \overline{A}\overline{C} + \overline{B}\overline{C} \\
 &= \overline{A} + \overline{A}\overline{C} + \overline{B}\overline{C} \\
 &= \overline{A}(1+C) + \overline{B}\overline{C} \\
 &= \overline{A} + \overline{B}\overline{C}
 \end{aligned}$$

Design an adder —

1. Half Adder
2. Full Adder

2-bit
Half Adder

Input		Output	
A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

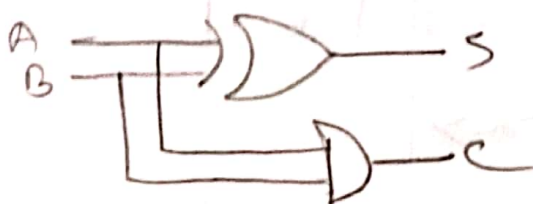

Half Adder

$$S = \overline{A}\overline{B} + \overline{A}B + A\overline{B} + AB = A \oplus B$$

$$C = AB$$

Full Adder	Input			Output	
	X	Y	Z	C	S
	0	0	0	0	0
	0	0	1	0	1
	0	1	0	0	1
	0	1	1	1	0
	1	0	0	0	1
	1	0	1	1	0
	1	1	0	1	0
	1	1	1	1	1

$$\text{Sum} = \Sigma(1, 2, 4, 7)$$

$$\text{Carry} = \Sigma(3, 5, 6, 7)$$

Sum

YZ

		00	01	11	10
X	0	0 ₀	1 ₁	0 ₃	1 ₂
	1	1 ₄	0 ₅	1 ₇	0 ₆

$$S = X\bar{Y}\bar{Z} + \bar{X}YZ + X\bar{Y}Z + \bar{X}Y\bar{Z}$$

Carry
YZ

		00	01	11	10
X	0	0 ₀	0 ₁	1 ₃	0 ₂
	1	0 ₄	1 ₅	1 ₇	1 ₆

$$C = YZ + XZ + XY$$

$$\begin{aligned}
 S &= x\bar{y}\bar{z} + \bar{x}\bar{y}z + x\bar{y}z + \bar{x}y\bar{z} \\
 &= x(\bar{y}\bar{z} + \bar{y}z) + \bar{x}(\bar{y}z + y\bar{z}) \\
 &= x(\overline{y \oplus z}) + \bar{x}(y \oplus z) \\
 &= x \oplus (y \oplus z)
 \end{aligned}$$

→ Full Adder using half Adder / carry look ahead Adder

Full Adder,

$$\begin{aligned}
 \text{Sum} &= A \oplus (B \oplus C) \\
 \text{Carry} &= AB + BC + CA
 \end{aligned}$$


Half Adder,

$$\begin{aligned}
 \text{Sum} &= A \oplus B \\
 \text{Carry} &= AB
 \end{aligned}$$

$$\text{Sum} = A \oplus X \quad [\text{let, } X = B \oplus C]$$

$$\text{Carry} = AB + BC + CA$$
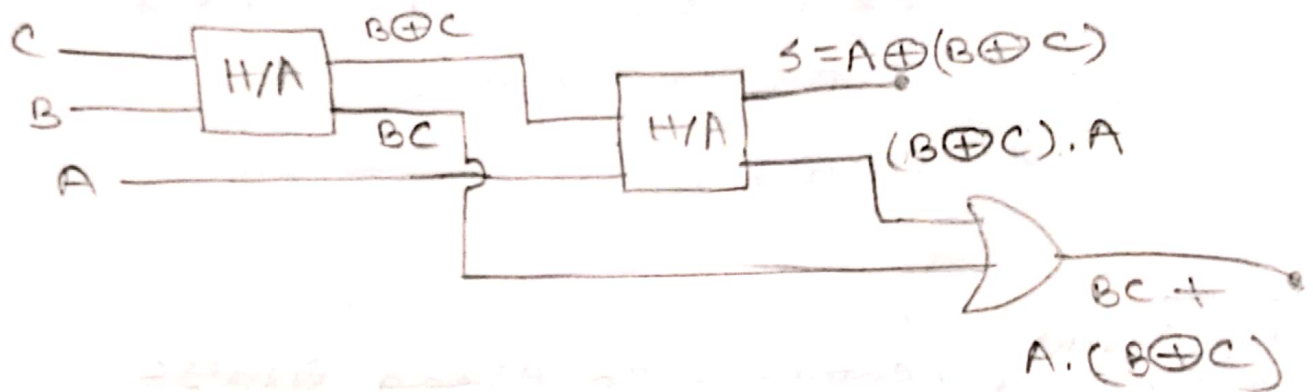
$$\begin{aligned}
 &= AB(C + \bar{C}) + BC(A + \bar{A}) + CA(B + \bar{B}) \\
 &= ABC + AB\bar{C} + ABC + \bar{A}BC + ABC + A\bar{B}C \\
 &= ABC + \bar{A}BC + A\bar{B}C + AB\bar{C} \\
 &= ABC + \bar{A}BC + A(\bar{B}C + B\bar{C}) \\
 &= \cancel{ABC} + \cancel{\bar{A}BC} = BC(A + \bar{A}) + A(\bar{B}C + B\bar{C}) \\
 &= BC + A(B \oplus C)
 \end{aligned}$$




Universal Adder (Addition Subtraction)
(parallel bit)

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

$$A - B =$$

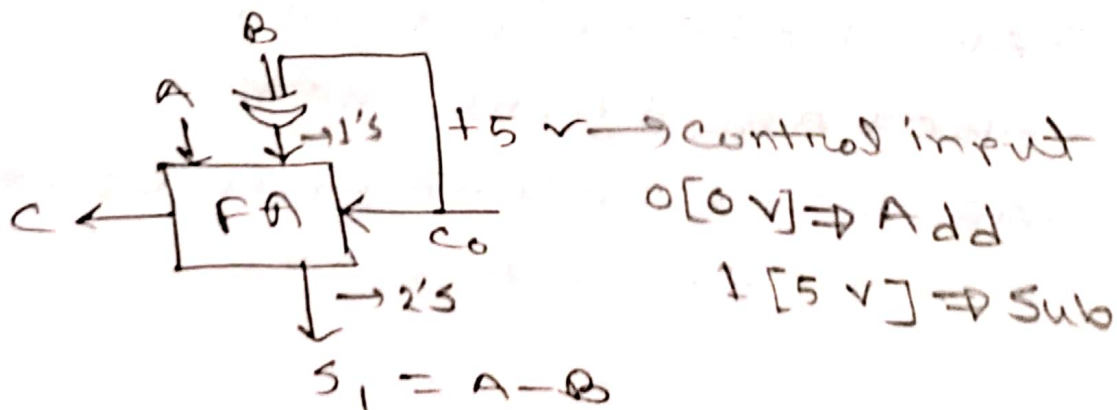

BCD AdderBCD $\rightarrow$ four bit representation

$$\begin{array}{ccc} 5 & 2 & 3 \\ \swarrow & | & \searrow \\ 0101 & 0010 & 0011 \end{array} \rightarrow (010100100011)_{BCD}$$

$23 \rightarrow 00100011$

$28 \rightarrow 00101000$

$51 \rightarrow 01001011 \rightarrow \text{greater than 9}$

$$\begin{array}{r} 01001011 \\ \quad \quad \quad \quad \quad + 0110 \rightarrow \text{correction factor} \\ \hline 01010001 \end{array}$$

5 1

highest decimal
1001 $\rightarrow$ 9

1's $\rightarrow$ 0110 $\rightarrow$ 6

1111 $\rightarrow$ 15
highest error

$$\begin{array}{r} \# \quad 238 \rightarrow 0010 \quad 0011 \quad 1000 \\ \quad 296 \rightarrow 0010 \quad 1001 \quad 0110 \\ \hline \quad 534 \quad \quad 0100 \quad 1100 \quad 1110 \\ \quad \quad \quad + 0110 \quad 0110 \\ \hline \quad \quad 0101 \quad 0011 \quad 0100 \\ \quad \quad \quad \downarrow \quad \quad \downarrow \quad \quad \downarrow \\ \quad \quad \quad 5 \quad \quad 3 \quad \quad 4 \end{array}$$

$$\begin{array}{r} \# \quad 6 \rightarrow 0110 \\ \quad 4 \rightarrow 0100 \\ \hline \quad 10 \rightarrow 1010 \rightarrow > 9 \\ \quad \quad + 0110 \\ \quad \quad \hline \quad \quad 10000 \end{array}$$

Book: Tucci, Morrison